



VRIJE
UNIVERSITEIT
BRUSSEL

Analog Electronics lab session

Alican, Gaurav, Lucas, Sriram, Thomas


Summary

- Session 2:
 - Cascade of common source amplifier stages
 - The two-stage amplifier with Miller compensation

Building some intuition

- Do exercise I
 - ETA: 10 minutes

EXERCISE 1-A

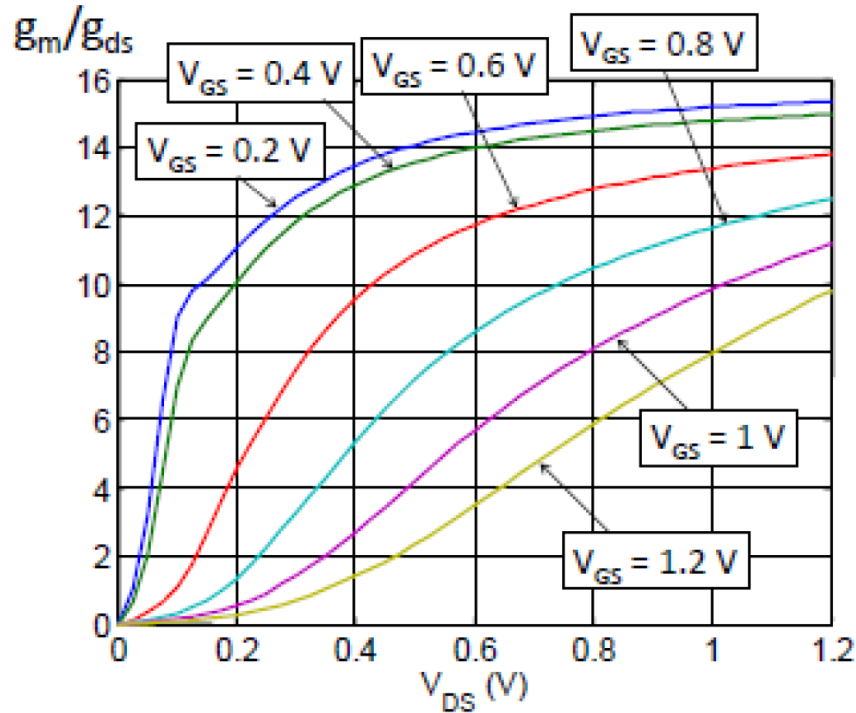

- For the high gain, the transistor should operate in the weak inversion ($V_{GS}=0.2\text{V}$).
- The V_{DS} needs to be increased in order to lower g_{ds} ($V_{DS}=1.2\text{V}$).
- According to curves, the highest gain we can get is around 15V/V .

EXERCISE I-B

$$f_T = \frac{g_m}{2\pi * (C_{gs} + C_{gd})}$$

- For the highest speed, V_{OV} should be the largest, so $V_{GS}=1.2\text{ V}$.
- In this case to get the highest gain, $V_{DS}=1.2\text{ V}$.
- In conclusion, the result is 10 V/V .


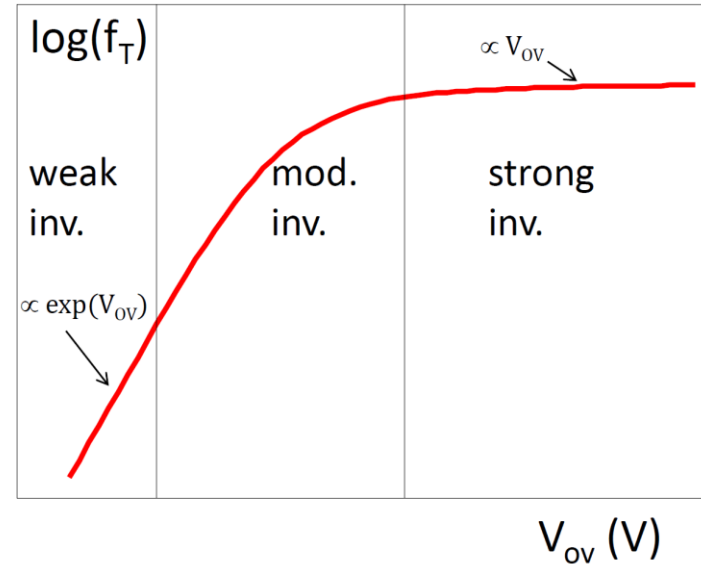


Figure 1.42: Dependence of f_T on the overdrive voltage.


EXERCISE I-C

- Cascade

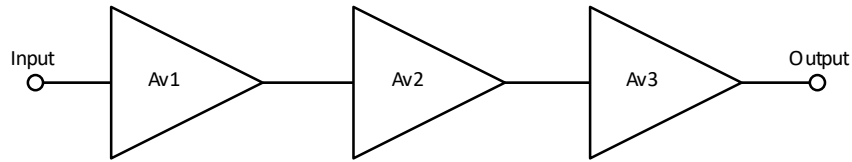

- $The\ total\ gain = A_{v1} * A_{v2} * A_{v3}$

- Cascode

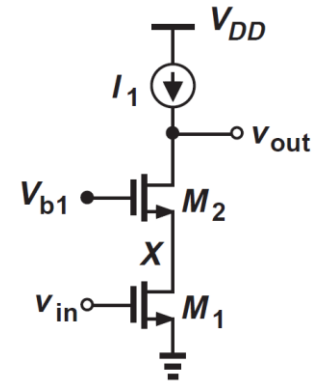


- $The\ gain = -\frac{g_{m1} * g_{m2}}{g_{ds1} * g_{ds2}}$

Building some intuition

- Do exercise 2
 - ETA: 25 minutes

EXERCISE 2-A

Finding the Total Gain

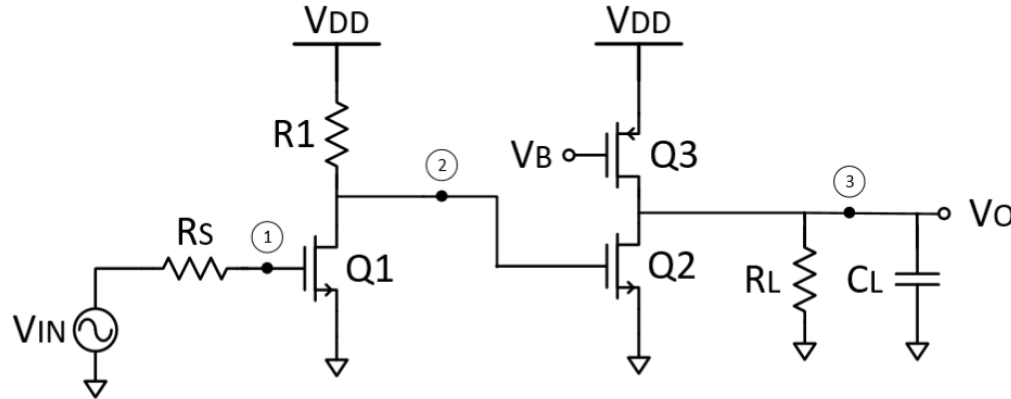


■ $\text{Gain} = \frac{V_0}{V_{in}} = \frac{I_0}{V_{in}} * \frac{V_0}{I_0} = G_m * R_{out}$

- $A_{v1} = -g_{m1} * R_1 = -2\text{mS} * 5\text{k}\Omega = -10\text{V/V}$
- $A_{v2} = -g_{m2} * R_L = -20\text{mS} * 500\Omega = -10\text{V/V}$
- $A_v = A_{v1} * A_{v2} = 100\text{ V/V} = 40\text{dB}$

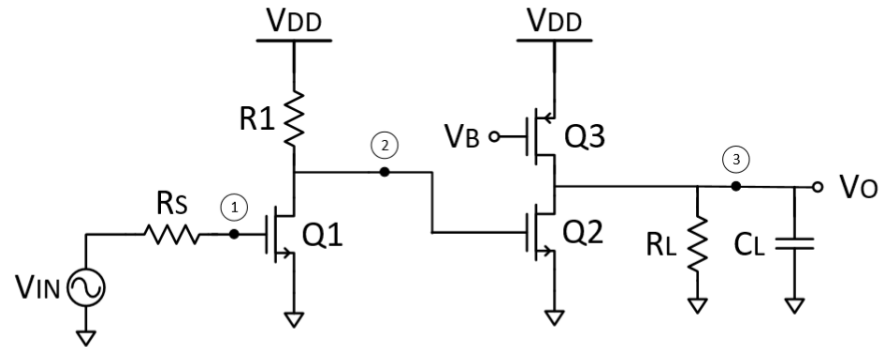EXERCISE 2-B

Finding Pole Frequencies


- $$\text{pole frequency at node } n \text{ in rad/s} = \frac{1}{\text{Total resistance between node } n \text{ and AC ground}} * \frac{1}{\text{Total capacitance between node } n \text{ and AC ground}}$$



- $$\omega_{p1} = \frac{1}{R_S * (C_{gs1} + C_{gd1} * (1 + g_{m1} * R_1))} = \frac{1}{500\Omega * 130fF} = 15.4G \text{ rad/s}$$
- $$\omega_{p2} = \frac{1}{R_1 * (C_{gs2} + C_{gd2} * (1 + g_{m2} * R_L))} = \frac{1}{5k\Omega * 195fF} = 1G \text{ rad/s}$$
- $$\omega_{p3} = \frac{1}{R_L * C_L} = \frac{1}{500\Omega * 1.1pF} = 1.8G \text{ rad/s}$$

EXERCISE 2-C


Finding ω_T Value

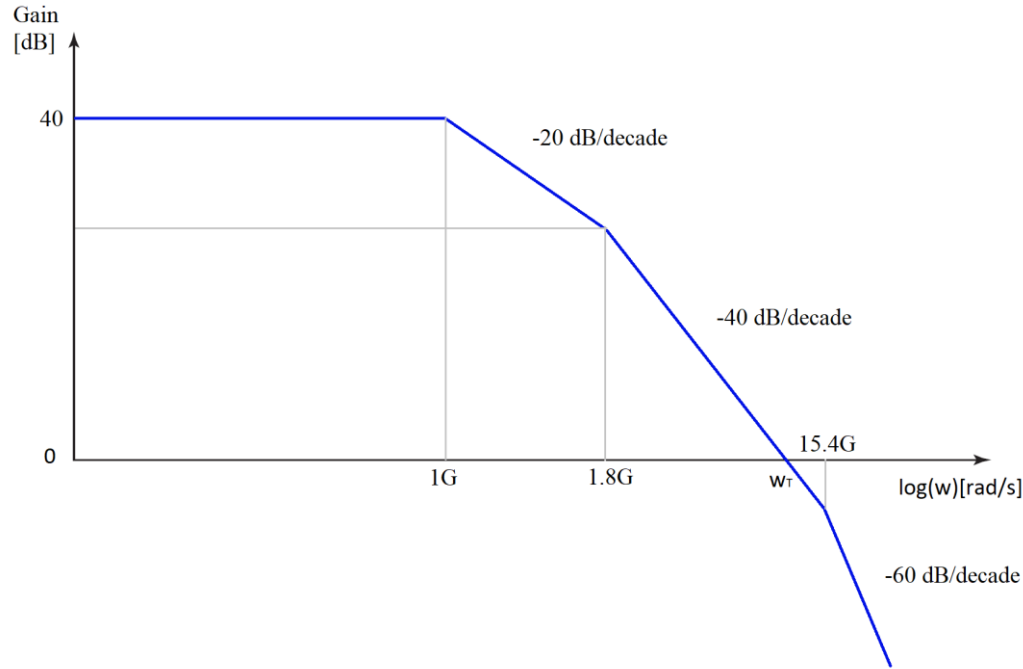

- $40 - 20 * \log\left(\frac{1.8G \text{ rad/s}}{1G \text{ rad/s}}\right) = 34.9dB$
- $34.9 - 40 * \log\left(\frac{\omega_T}{1.8G \text{ rad/s}}\right) = 0dB$
- $\omega_T = 13.4G \text{ rad/s}$

EXERCISE 2-C


Asymptotic Bode Approximation vs Exact Curve

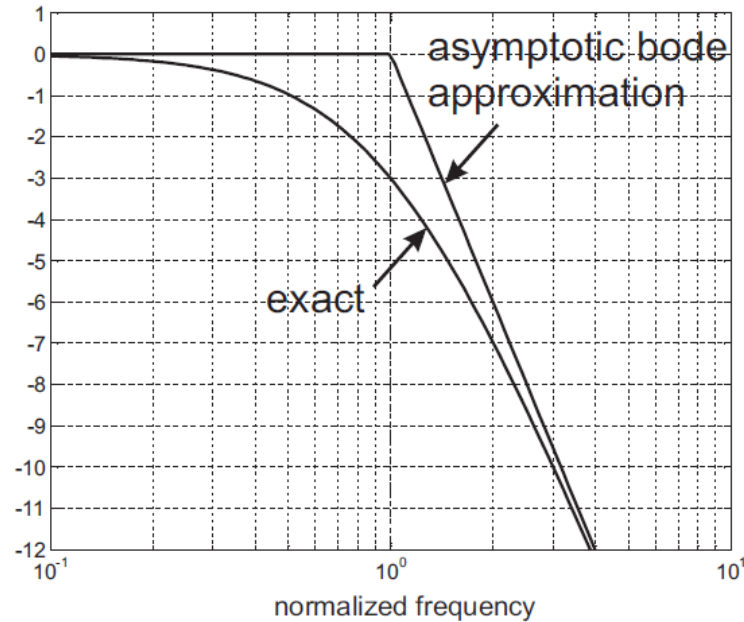

EXERCISE 2-C


MATLAB Magnitude Plot

- Calculated $\omega_T = 13.4G \text{ rad/s}$

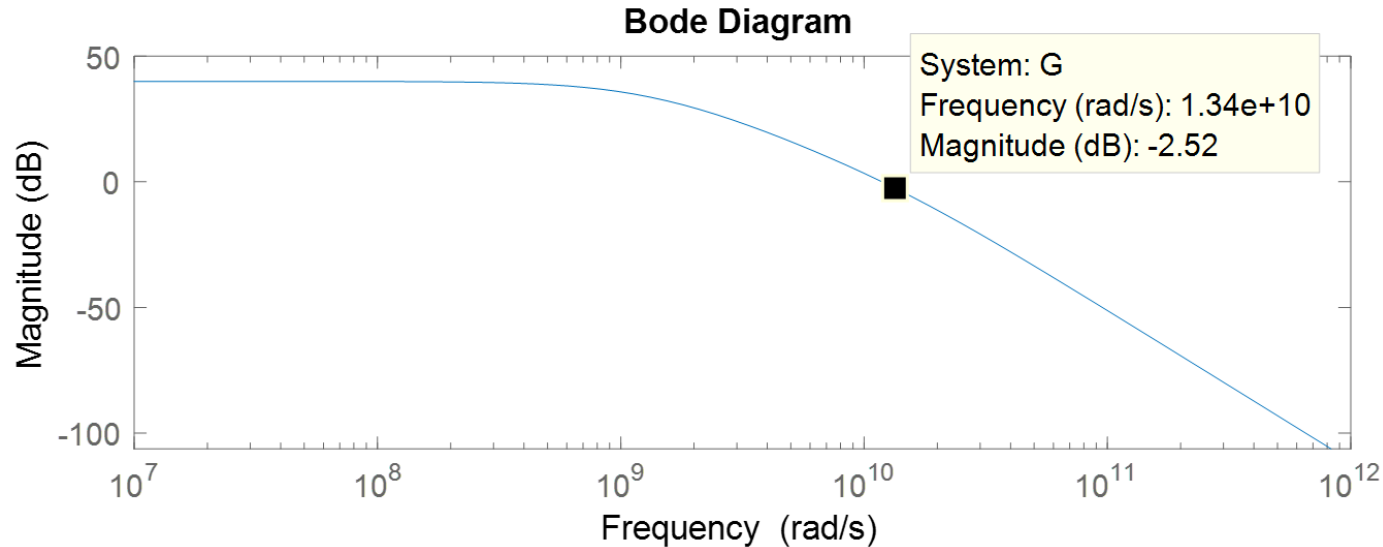


EXERCISE 2-C

Phase Shift due to Poles and Zeros

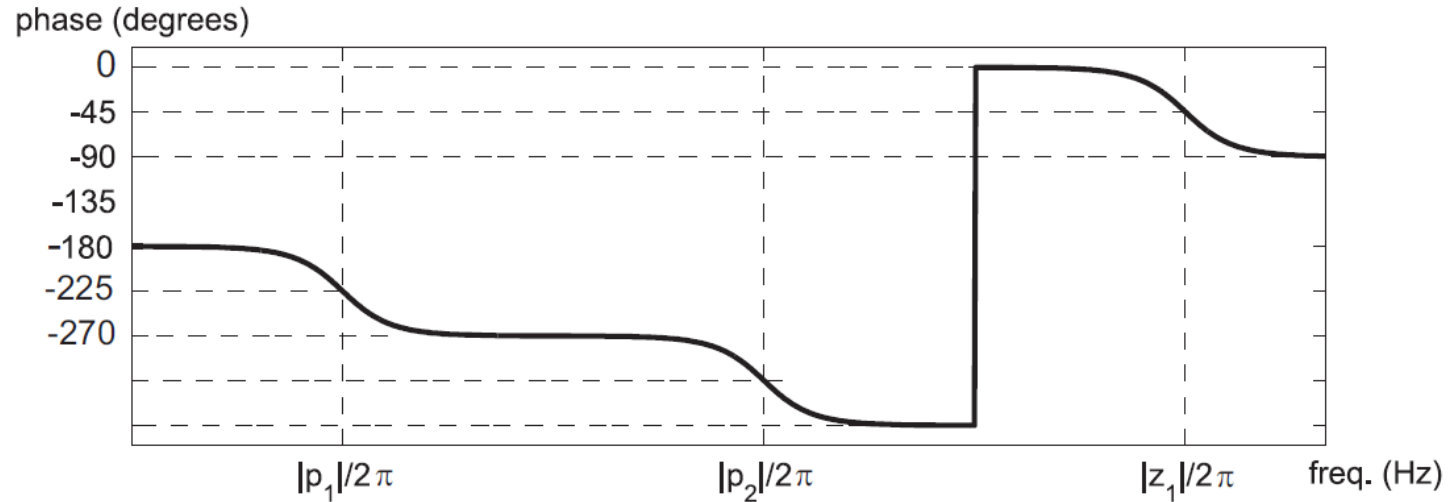

EXERCISE 2-C


MATLAB Phase Plot

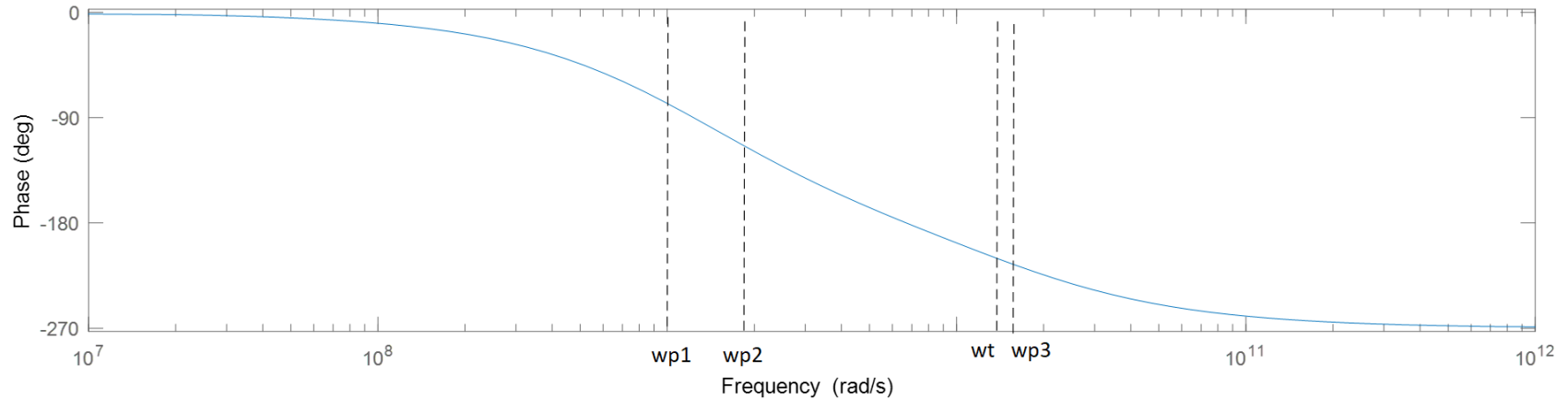


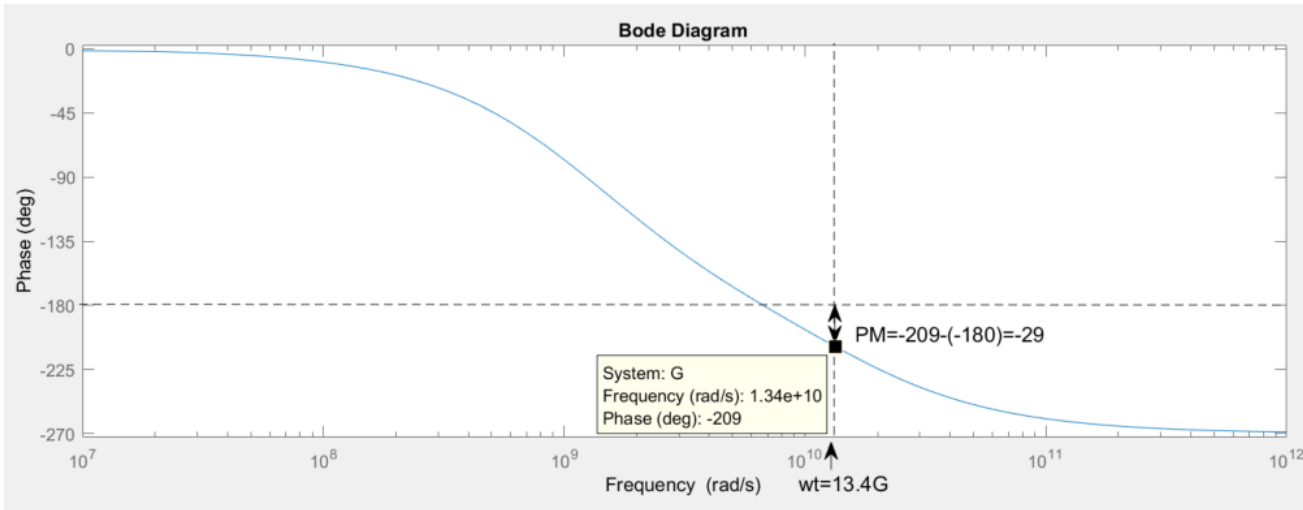
EXERCISE 2-C

Finding Phase Margin

- $Total\ phase\ shift = 0 - \tan^{-1} \frac{13.4 Grad/s}{1 Grad/s} - \tan^{-1} \frac{13.4 Grad/s}{1.8 Grad/s} - \tan^{-1} \frac{13.4 Grad/s}{15.4 Grad/s} = -209.1^\circ$
- $Phase\ margin = -209.1^\circ - (-180^\circ) = -29.1^\circ$



DERIVING REAL ZEROS

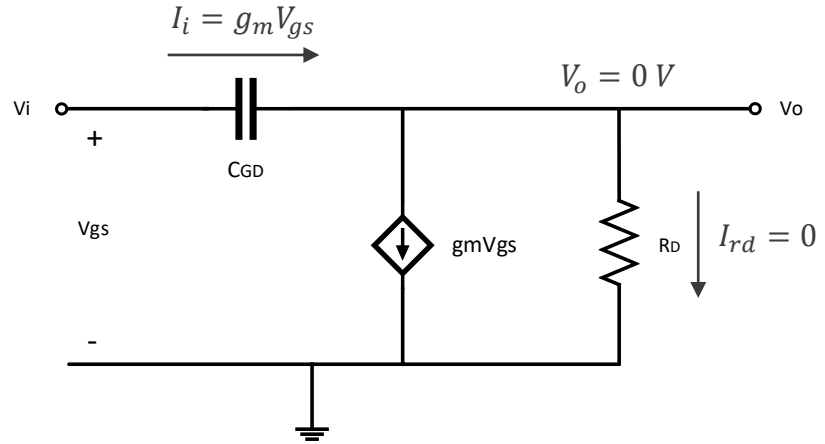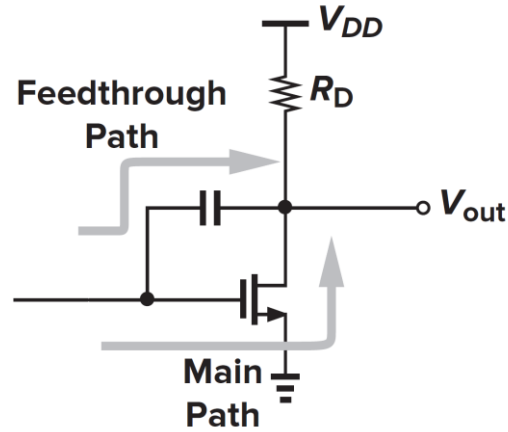

- $\frac{V_i}{1/(s_z * C_{GD})} = g_m * V_i$
- $s_z = \frac{g_m}{C_{GD}}$

Building some intuition

- Do exercise 3
 - ETA: 25 minutes

EXERCISE 3-A

Dependence of Poles on C_{gd} value


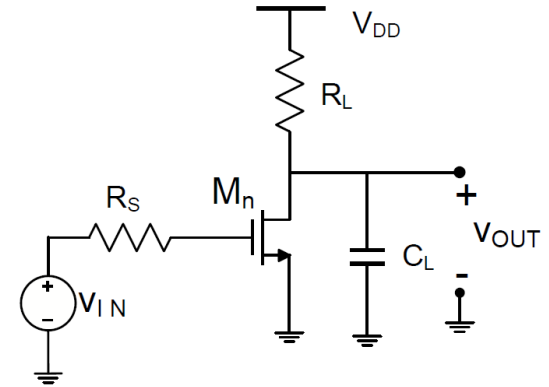
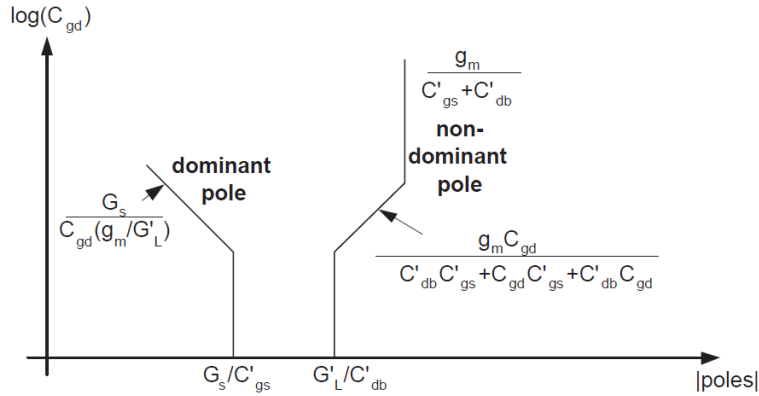


Figure 2.15: Bode diagram of pole splitting: asymptotes indicate the position of poles as a function of C_{gd} on a log-log scale.

- $C'_{gs} = C_{gs} + C_{gb}$
- $C'_{db} = C_{db} + C_L$
- $G'_L = g_{ds} + G_L$

EXERCISE 3-A


Finding the Value of C_c

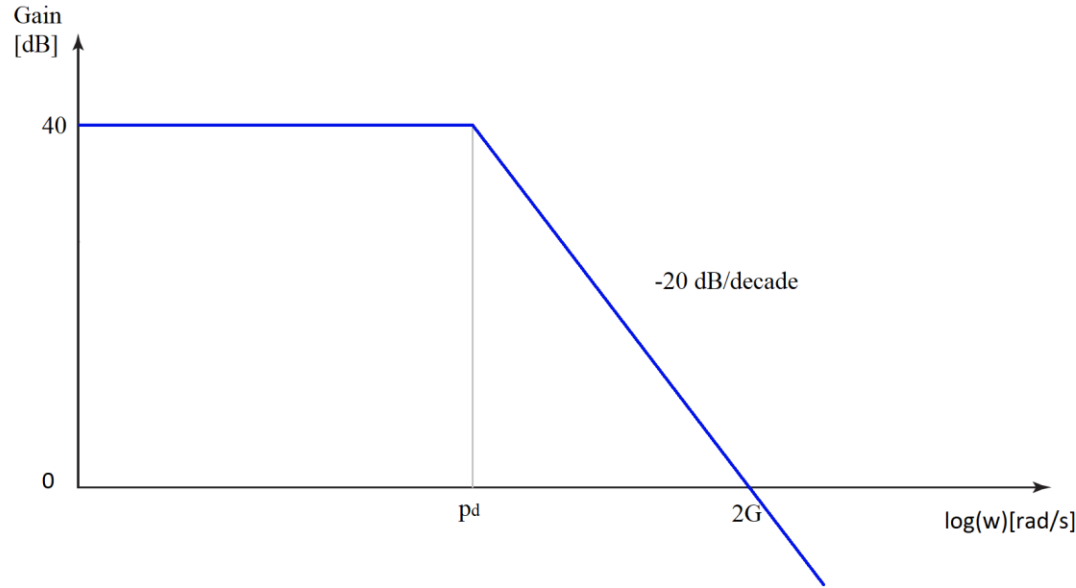

- $\omega_T = GBW = |A_v * p_d|$
- $A_v = g_{m1} * R_1 * g_{m2} * R_L$
- $p_d = \frac{-1}{R_1 * (C_c * g_{m2} * R_L)}$
- $\omega_T = GBW = |A_v * p_d| = \frac{g_{m1}}{C_c}$
- $\omega_T = 2Grad/s = \frac{2mS}{C_c}$
- $C_c = 1pF$

EXERCISE 3-B

Finding Pole Frequencies

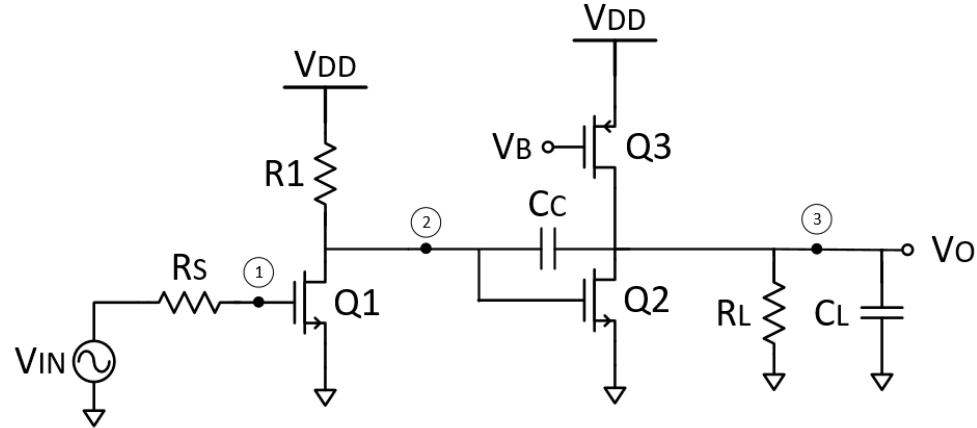


- $\omega_{p1} = \frac{1}{R_S*(C_{gs1}+C_{gd1}*(1+g_{m1}*R_1))} = \frac{1}{500\Omega*130fF} = 15.4G rad/s$
- $\omega_{p2} = \frac{1}{R_1*(C_c*g_{m2}*R_L)} = \frac{1}{5k\Omega*20mS*500\Omega*1pF} = 20M rad/s$
- $\omega_{p3} = \frac{g_{m2}}{C_L} = \frac{20mS}{1.1pF} = 18.2G rad/s$
- $\omega_{z1} = \frac{g_{m2}}{C_c} = \frac{20mS}{1pF} = 20G rad/s$

EXERCISE 3-B

MATLAB Magnitude Plot


- Calculated $\omega_T = 2G \text{ rad/s}$

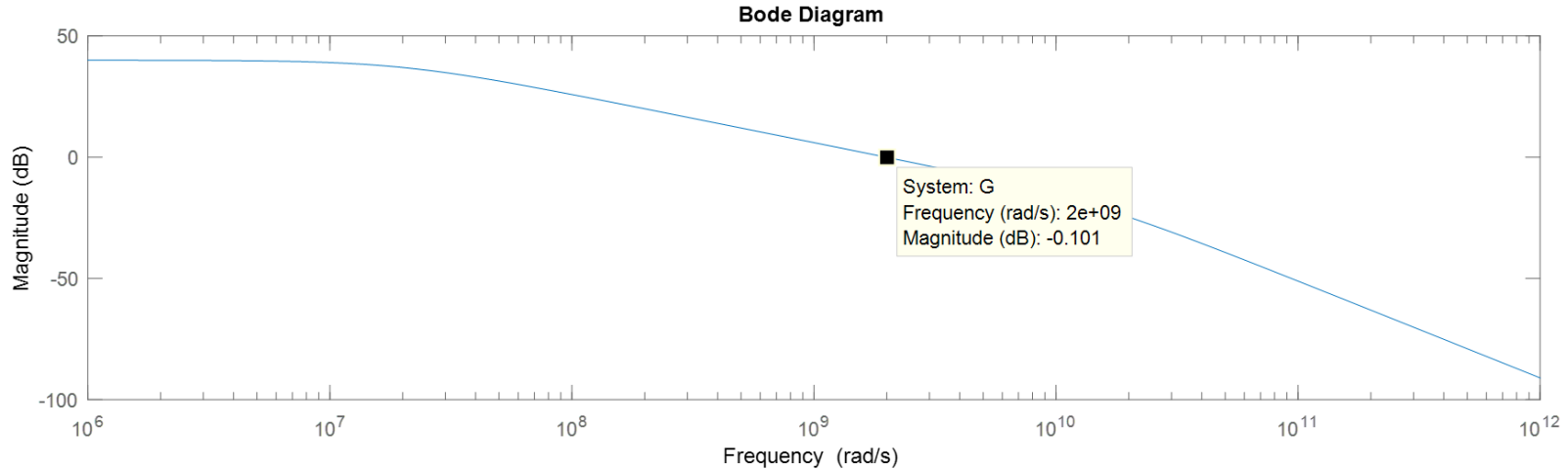

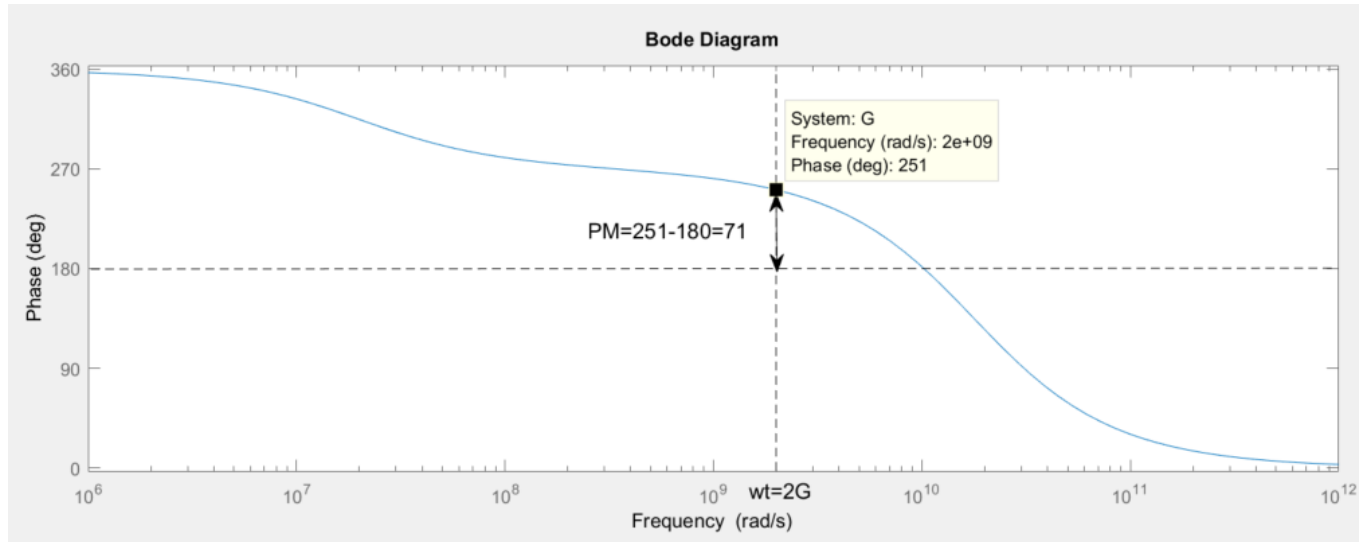EXERCISE 3-B

Finding Phase Margin

- $Total\ phase\ shift = 0 - \tan^{-1} \frac{2Grad/s}{20Mrad/s} - \tan^{-1} \frac{2Grad/s}{15.4Grad/s} - \tan^{-1} \frac{2Grad/s}{18.2Grad/s} - \tan^{-1} \frac{2Grad/s}{20Grad/s} = -108.8^\circ$
- $Phase\ margin = -108.8^\circ - (-180^\circ) = 71.2^\circ$




Building some intuition

- Do exercise 4
 - ETA: 15 minutes

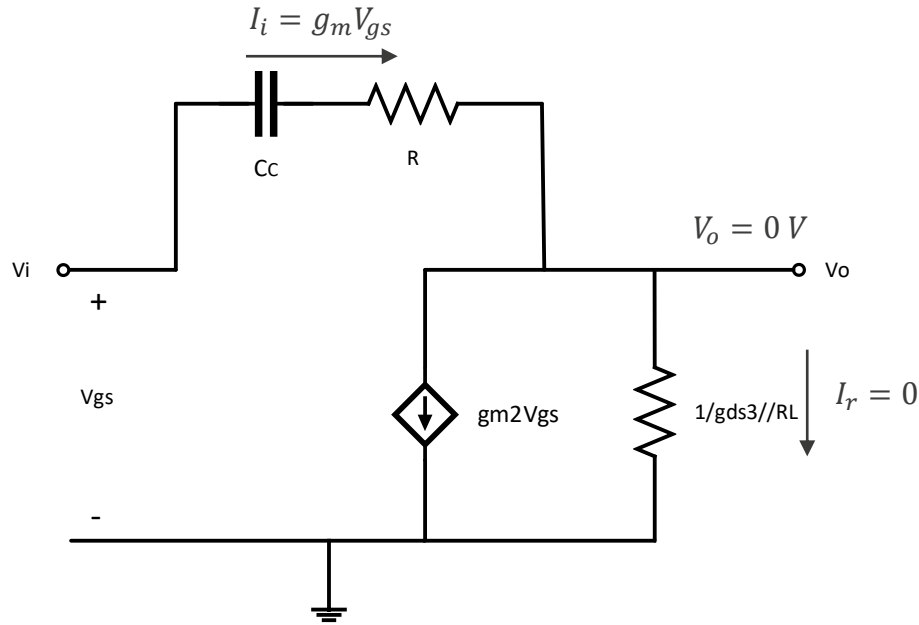EXERCISE 4-A

Expression of the Zero After Adding the Resistor



- $$\frac{V_i}{R + \frac{1}{s_Z C_c}} = g_{m2} * V_i$$
- $$s_Z = \frac{1}{C_c * (\frac{1}{g_{m2}} - R)}$$

EXERCISE 4-A

Finding Value of R

- $\omega_{z1} = \omega_{p1} = 15.4 \text{ Grad/s} = \left| \frac{1}{C_c * \left(\frac{1}{g_{m2}} - R \right)} \right|$
- $R = 64.9 \Omega$

EXERCISE 4-B

Finding Phase Margin

- $Total\ phase\ shift = 0 - \tan^{-1} \frac{2Grad/s}{20Mrad/s} - \tan^{-1} \frac{2Grad/s}{18.2Grad/s} = -95.7^\circ$
- $Phase\ margin = -95.7^\circ - (-180^\circ) = 84.3^\circ$

FINAL REMARK

$|p_2|/GBW_T$ vs Phase Margin in Two-poles System

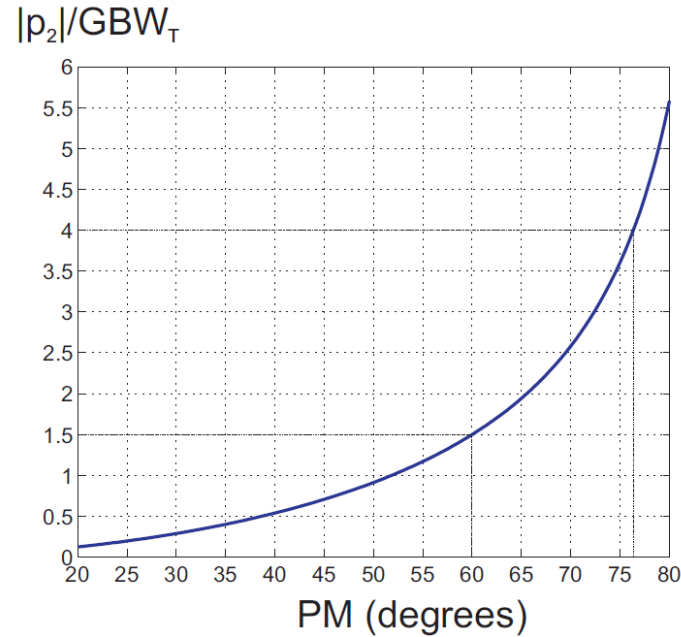


Figure 7.3: Relation between the phase margin and the ratio of the second pole and GBW_T .



embracing a better life