



VRIJE
UNIVERSITEIT
BRUSSEL

Analog Electronics lab session

Alican, Guarav, Lucas, Sriram, Thomas

The TA team



Lucas Santana
Master's in Aeronautics Institute of Technology (Brazil, 2019)
Works with delta sigma analog to digital converters



Alican Çağlar
Master's in Istanbul Technical University (Turkey, 2019)
Works with readout circuits for quantum computing



Thomas Gorzka
Master's in RWTH Aachen (Germany, 2019)
Works with transceiver circuits for optical and wireline communication



Sriram Balamurali
Master's in TU Delft (The Netherlands, 2019)
Works with millimeter wave frequency generation



Guarav Agrawal
Master's in IIT Madras (India, 2015)
Works with millimeter wave transceivers for high-speed wireless communications

- Session 1: essentials of the MOS transistor
- Session 2: cascade of CS amplifier stages and Miller compensation
- Session 3: design of differential pairs and of an OTA
- Session 4: notions of noise in circuits

Summary

- Session I:
 - How to use the Matlab and the LTSpice tool
 - MOS design curves and trade-offs
 - Common source amplifier with resistive load
 - Common source amplifier with PMOS load

Core differences between lectures and lab classes

■ Lectures:

- Analysis of given architectures
- Modeling of transistors and complex circuits
- Finding equations for performance parameters (gain, bandwidth, power,...)


Common-source amplifier

$$A_v = -g_m(R_L || r_{ds})$$

$$A_i = g_m / sC_{gs}$$


$$\frac{i_{out}}{V_{in}} = g_m$$

$$C_{in} = C_{gs} + C_{gd}(1 - A_v)$$

 


■ Lab:

 
- Quantitative design of the known architectures
- How to size and bias a transistor (W, L, V_{gs}, V_{ds}) to achieve a certain performance using Matlab
- How to simulate a circuit using SPICE to validate the correctness of design



How does the Design process work

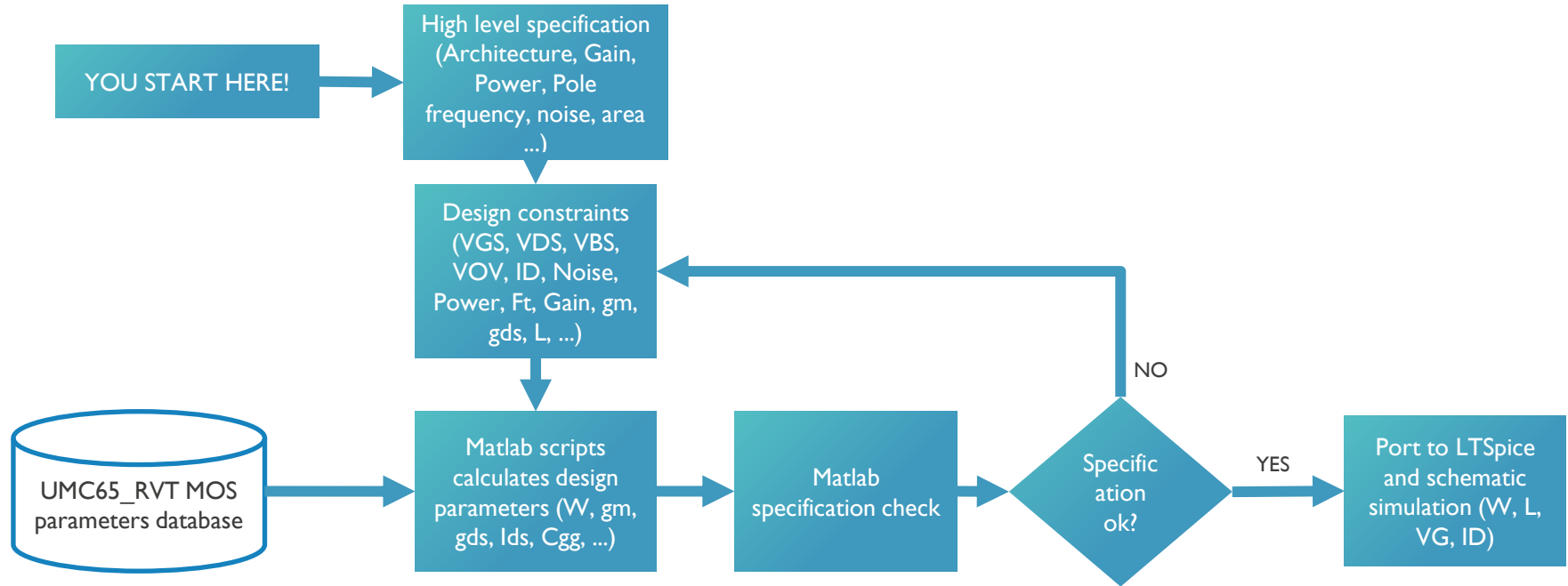

How does the design process work


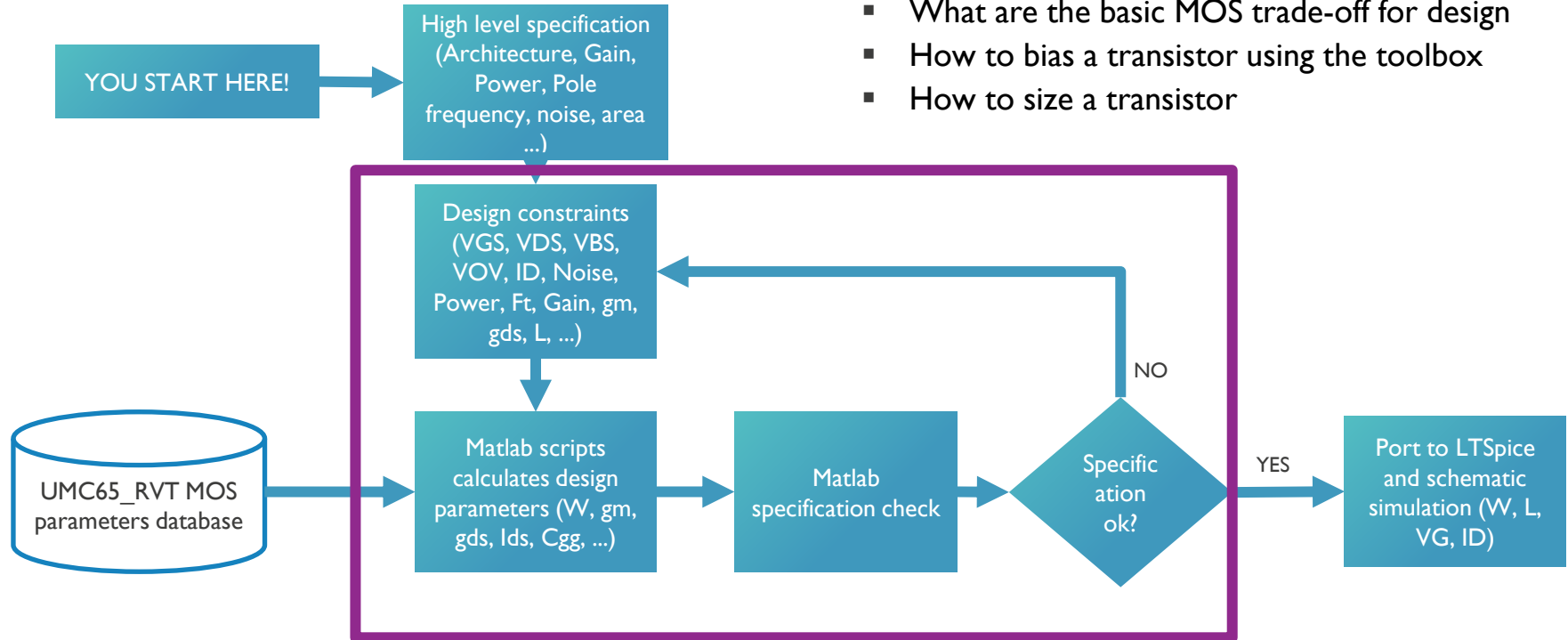


- What do you need to understand after this class?
 - What are the basic MOS trade-off for design
 - How to bias a transistor using the toolbox
 - How to size a transistor

Building some intuition


- Do exercise 1 and exercise 2
 - ETA: 15 minutes

Exercise I

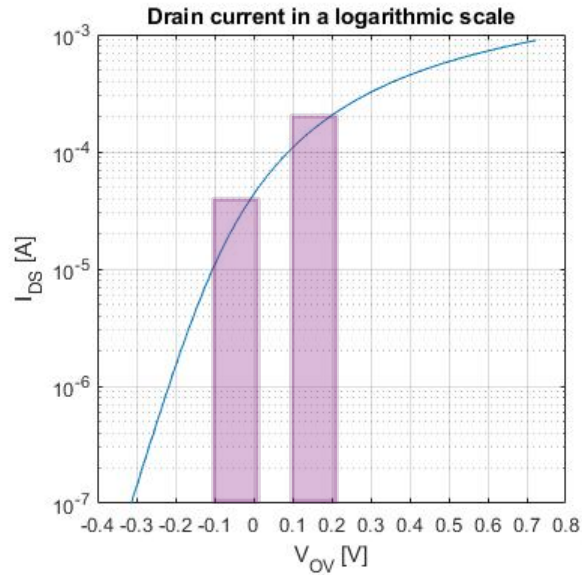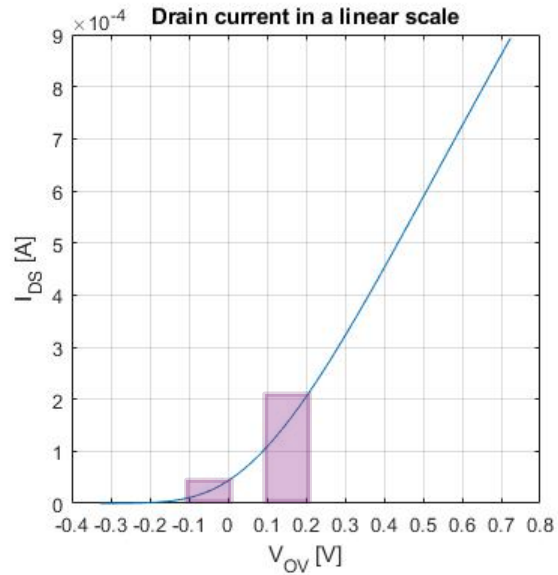

- WI: $v_{ov} < -0.1V$ or **0V**
- MI: $-0.1V$ or **0V** $< v_{ov} < 0.2V$ or $0.3V$
- SI: $v_{ov} > 0.2V$ or $0.3V$

Exercise 2

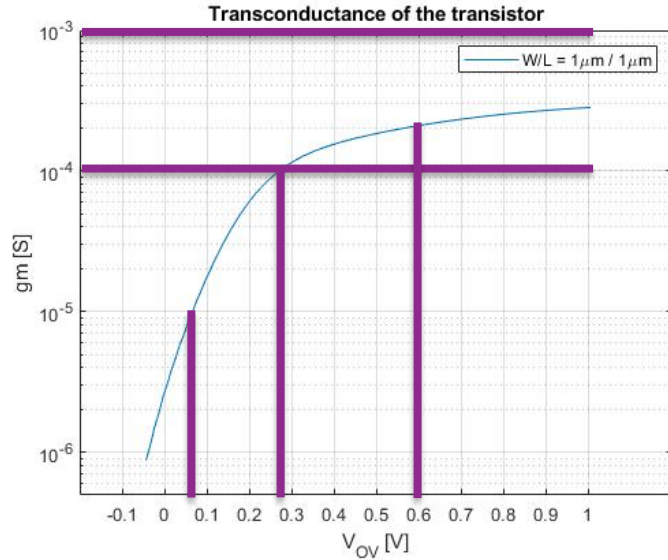

- 0.1 mS
 - Directly from the graph: $v_{ov} = 0.3V \rightarrow V_{GS} = 0.6V$
- 1 mS – multiple choices
 - Take 10x 0.1 mS in parallel with $V_{GS} = 0.6V$
 - Take 5x 0.2 mS in parallel with $V_{GS} = 0.9V$
 - Take 100 x 0.01 mS in parallel with $V_{GS} = 0.35V$

What does a Matlab code looks like

housekeeping

```
32 %% Adding paths + Loading MOS tables
33 addpath(genpath('circuitDesign'));
34 addpath(genpath('functions'));
35 addpath(genpath('models'));
36
37 w = warning ('off','all'); % Turn off warnings
38
39 clear;
40 close all;
41 clc;
42
43 load ('UMC65_RVT.mat');
```

■ Loading functions and .mat file

```
45 %% Initialize everything
46 designkitName = 'umc65';
47 circuitTitle = 'Analog Design - Session 1';
48
49 %Declaration of the circuit components
50 elementList.nmos = {'Mn1','Mn2','Mn3','Mn4'};
51 elementList.pmos = {};
```

■ Defining the transistors used in the circuit (Mn is a struct with the transistor parameters as fields)

```
53 spec.VDD = 1.1;
54 choice.maxFingerWidth = 10e-6;
55 choice.minFingerWidth = 200e-9;
56 simulator = 'spectre';
57 simulFile = 0;
58 simulSkelFile = 0;
59 analog = cirInit('analog', circuitTitle, 'top', elementList, spec, choice,...
60 designkitName, NRVT, PRVT, simulator, simulFile, simulSkelFile);
61
62 analog = cirCheckInChoice(analog, choice);
63
```

■ Defining technology constraints

Plotting the MOS IDS curves

Session I_part I.m

```
%% Circuit
disp('      Vd      ');
disp('      |      ');
disp('  Vg---Mnx      ');
disp('      |      ');
disp('      Vs      ');

fprintf('\n--- First Exercise: Designing transistor from scratch ---\n');
```

- Fixed parameters: W, L
- Sweep parameters: V_{GS}, V_{DS}
- Calculated parameters: I_{DS} (to be plot), V_{TH} (byproduct of bias point) and other Operating point parameters (g_m, g_{ds}, \dots)

Writing the code together

Useful functions

tableValueWref

tableValueWref retrieving the value of an intrinsic MOS parameter for the reference width, directly from a given table.

`RESULT = mosIntValueWref(PARAM, TABLE, LENGTH, VGS, VDS, VSB)` returns the value of the MOS operating point parameter `PARAM` (specified as a string) for a given `TABLE`.
`PARAM` must exist as a field of the given `TABLE`.
Possible names for `PARAM` can be found by running `tableDisplay(TABLE)`.

EXAMPLE :

```
id = tableValueWref('ids', N, 0.18e-6, 0.7, vdd/2, 0)
```

mosNfingers

mosNfingers computation of the number of fingers for a MOS transistor.

mosOpValues

mosOpValues computation of all operating parameters of a MOS transistor

`MOS = mosOpValues(MOS)` computes the value of intrinsic and extrinsic operating point parameters (in S.I. units) of a given transistor `MOS`. The datastructure of the transistor which is specified as an argument is also returned. However, after this function has returned, all fields of the transistor related to intrinsic and extrinsic operating point parameters have been added to the datastructure of the transistor. Existing extrinsic geometry parameters are NOT recomputed. Also, the values of `vgb`, `vgd` and `vdb` are computed (or updated) from `vgs`, `vds` and `vsb`.

EXAMPLE :

```
Mn1 = mosOpValues(Mn1)
```

- To extract the VTH value (weak dependency with MOS W)
- To slice the Width according to the maximum desired finger width
- To calculate all the other MOS parameters, in this case it is mainly Mn.ids

Analysis


- IDS graph
 - Reset to X-Z view: which regions can you see?
 - Reset to Y-Z view: which regions can you see?
- MOS saturation graph
 - Reset to Y-X view: can you discuss about the trends in V_{dsat} (V_{ds} after which the transistor is in saturation)?

Building some intuition

- Exercise 3 and 4
 - ETA: 15 minutes



Exercise 3

Required width for a $g_m = 1\text{mS}$

 

- Assuming $g_m = W \times f(\text{CMOS Parameters Constant})$
 - $WI: V_{OV} = -0.05\text{V} \rightarrow W = 1000\mu\text{m}@1\text{mS} \rightarrow W = 10000\mu\text{m}@10\text{mS}$
 - $MI: V_{OV} = 0.1\text{V} \rightarrow W = 50\mu\text{m}@1\text{mS} \rightarrow W = 500\mu\text{m}@10\text{mS}$
 - $SI: V_{OV} = 0.5\text{V} \rightarrow W = 5\mu\text{m}@1\text{mS} \rightarrow W = 50\mu\text{m}@10\text{mS}$

Exercise 4 - A

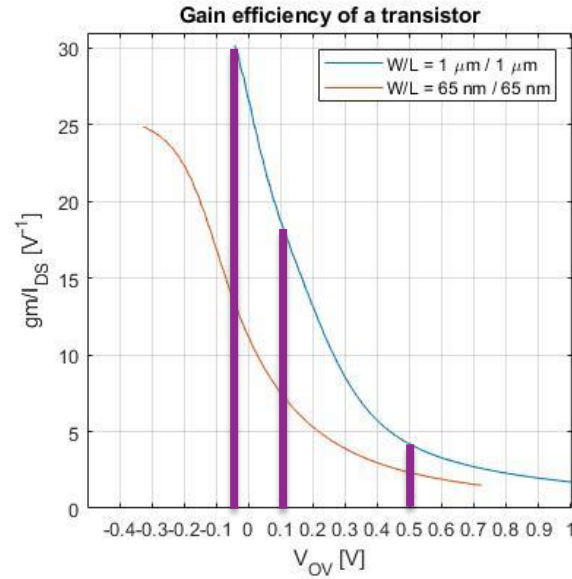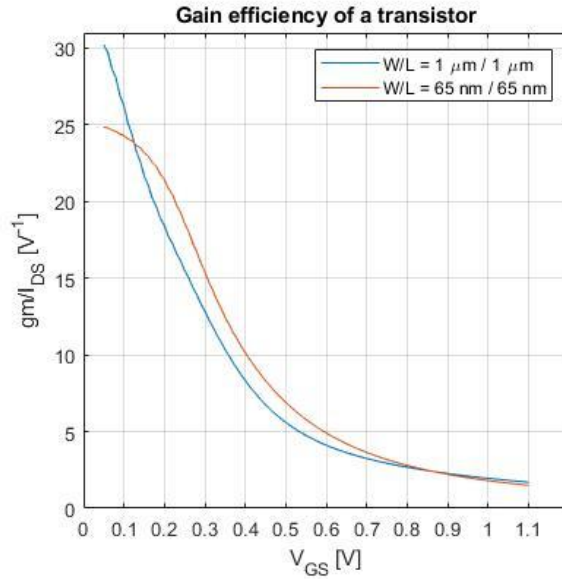

- Assuming $gm = 10mS$ from the previous exercise
 - $WI: V_{OV} = -0.05V \rightarrow \frac{gm}{I_{DS}} = 31 \rightarrow I_{DS} = 322\mu A$
 - $MI: V_{OV} = 0.1V \rightarrow \frac{gm}{I_{DS}} = 18 \rightarrow I_{DS} = 555\mu A$
 - $SI: V_{OV} = 0.5V \rightarrow \frac{gm}{I_{DS}} = 4 \rightarrow I_{DS} = 2500\mu A$

Exercise 4 - B

- Gain $A_V = g_m \times R_L$
- Voltage at Drain $V_{DS} = V_{DD} - R_L \times I_{DS}$
- Assuming an overdrive voltage of 0.1V
 - $V_{DS} = 1.0V \rightarrow R_L = \frac{1.1V - 1.0V}{555\mu A} = 180\Omega \rightarrow A_V = 1.8 \frac{V}{V}$
 - $V_{DS} = 0.55V \rightarrow R_L = \frac{1.1V - 0.55V}{555\mu A} = 990\Omega \rightarrow A_V = 9.9 \frac{V}{V}$
 - $V_{DS} = 0.2V \rightarrow R_L = \frac{1.1V - 0.2V}{555\mu A} = 1.62k\Omega \rightarrow A_V = 16.2 \frac{V}{V}$
 - General case: $A_V = g_m \times R_L = g_m \times \frac{V_{DD} - V_{DS}}{I_{DS}} = \frac{g_m}{I_{DS}} \times (V_{DD} - V_{DS})$, so the smaller the drain voltage the higher the gain, but at what cost?

Comparison table

Implementing the same $g_m = 10\text{mS}$	Width \propto Area	$I_{DS} \propto$ Power	Voltage gain $g_m R_L$ @ $V_{DS} = 0.55\text{V}$
Weak inversion ($v_{ov} = -0.05$)	10000 μm	370 μA	17.0 V/V (24.6dB)
Moderate inversion ($v_{ov} = 0.1$)	500 μm	714 μA	9.9 V/V (19.9dB)
Strong inversion ($v_{ov} = 0.5\text{V}$)	50 μm	1100 μA	2.2 V/V (6.8dB)

Plotting dependency to Channel length

Extracting small signal parameters: session1_part2.m

```
%% Circuit
disp('      spec.VDD/2      ');
disp('      |              ');
disp('      |              ');
disp('  Vg---Mnx              ');
disp('      |              ');
disp('      Vs              ');

fprintf('\n--- First Exercise: Designing transistor from scratch ---\n');
```

- Fixed parameters: V_{DS} , W/L
- Sweep parameters: L , V_{GS}
- Calculated parameters: g_m , g_{ds} , g_m/I_D (efficiency), g_m/g_{ds} (self gain)

Think about it!

- Extract the cutoff frequency (Mn.ft) value and plot alongside the previous graphs
 - For higher ft which length and inversion region are preferable?

Resistive load common source stage

```
%% EX1: Circuit
disp('      VDD      ');
disp('      |      ');
disp('      RL      ');
disp('      |-----OUT ');
disp('  IN---Mn1  |      ');
disp('      |      CL      ');
disp('      |      |      ');
disp('      GND  GND      ');
```

- Specification: Gain ($> 18\text{dB}$), GBW ($> 100\text{MHz}$) and Load (1pF) (given by system level decisions)
- Design choices: L , inversion region ($\text{VOV} = V_{\text{GS}} - V_{\text{TH}}$)
- Useful equations: $g_m = 2\pi \times \text{GBW} \times C_{\text{load}}$ (note that g_m turns to be a specification),

$$A_v = \frac{g_m}{g_{ds} + 1/R_L}$$


Writing the matlab code

1. $GBW = 100\text{MHz}$, $CL = 1\text{pF}$, $\text{Gain} > 18\text{dB}$, $\text{Width} < 1\text{mm}$
2. Calculate target gm from CL and GBW
3. Set your design choices ($Mn.lg$, $Mn.vov$)
4. Set the terminal voltages ($Mn.vds$, $Mn.vsb$, $VD = VDD/2$)
5. Extract V_{TH}
6. Set gate voltage ($Mn.vgs = V_{OV} + V_{TH}$)
7. Calculate width to realize given gm ($Mn.w = \text{mosWidth}('gm', \text{spec.gm}, Mn)$)
8. Extract IDS from mosOpValues
9. Calculate RL from IDS and VD
10. Calculate gain (equation in previous slide)
 - If the specification was met the design is ready to go to Cadence, if not go back to your design choices (lg and VOV) and start again reasoning towards which direction you want to go (long x short channel; weak x strong inversion)

Building some intuition



- Exercise 5:
 - ETA: 15 minutes

Exercise 5

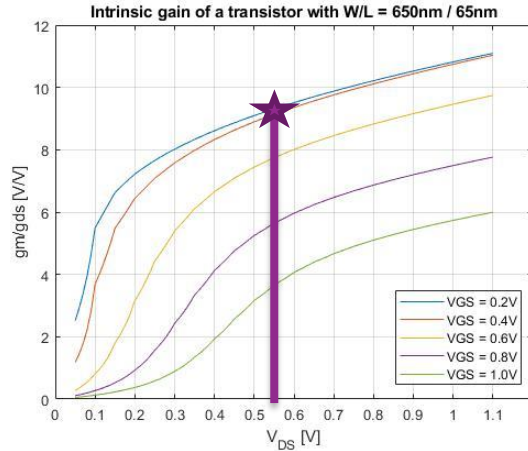

$$A_V = \frac{gm_{NMOS}}{gds_{NMOS} + gds_{PMOS}}$$

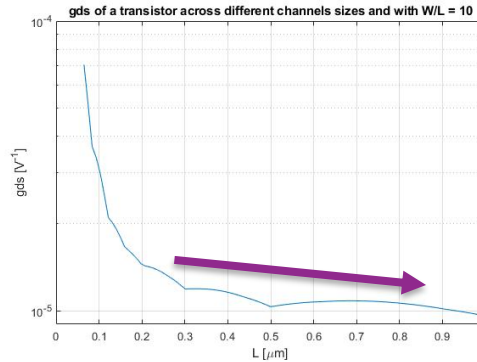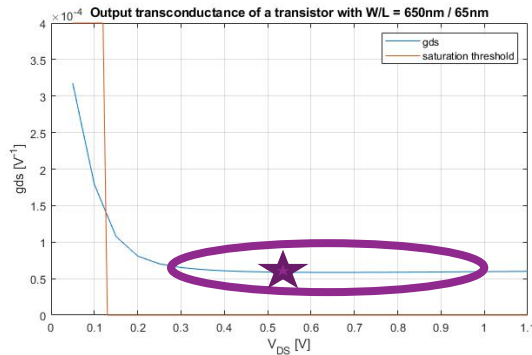$\frac{gm_{NMOS}}{gds_{NMOS}}$ maximization assuming the PMOS was already minimized



gds_{PMOS} minimization

PMOS load common source stage

```
%% EX2: Circuit
disp('      VDD      ');
disp('      |      ');
disp('      Mp2      ');
disp('      |-----OUT ');
disp(' IN---Mn2 |      ');
disp('      |   CL      ');
disp('      |   |      ');
disp('      GND GND      ');
```

- Specification: Gain (>26dB), GBW (>100MHz) and Load (1pF)

- Gain definition: $A_v = \frac{g_m^N}{g_{ds}^N + g_{ds}^P}$

Writing the Matlab code

1. GBW = 100MHz, CL = 1pF, **Gain > 26dB**, Width < 1mm
2. NMOS design has the same process as the case before
3. Sizing the PMOS load has some hard constraints
 1. $M_p.v_{ds} + M_n.v_{ds} = \text{spec.vdd}$ (forced by supply)
 2. $M_p.i_{ds} = M_n.i_{ds}$ (to provide a load functionality)
4. PMOS width is calculated based on its required IDS ($M_p.i_{ds} = \text{mosWidth('ids', } M_p.i_{ds}, M_p))$)

Testing the results in LTSPICE

homework

```
fprintf('\n--- Homework 1: Common source amplifier with cascodes ---\n');  
  
%% HW1: Circuit  
disp('      VDD      ');  
disp('      |      ');  
disp('  IN--Mp3      ');  
disp('      |      ');  
disp('      Mp4      ');  
disp('      |      ');  
disp('  +----+--OUT  ');  
disp('      |      ');  
disp('  Mn4 |      ');  
disp('      | CL      ');  
disp('  Mn3 |      ');  
disp('      |      ');  
disp('      GND GND  ');  
  
%% HW1: Specs  
spec.fGBW      = 80e6;    % [Hz] GBW frequency  
spec.Cl        = 15e-12;  % [F] load capacitance  
spec.VDD       = 1.1;    % [V] Power supply voltage  
spec.Vswing    = 0.2;    % [V] minimum peak to peak voltage swing of output  
bodyeffecton   = 1;
```

- Gain > 40dB
- Bodyeffecton triggers the body effect during biasing and calculations
 - This affects mainly the variation of V_{th} with respect to the V_{sb} voltage
 - Long channel devices suffer less from this effect than short channel devices



imec

embracing a better life